 



# Reading 14

## 15.4 FSMs to circuits (design)

- An FSM converts to a sequential circuit known as a controller, consisting of a register and combinational logic.
- A state register is the register in a controller, holding an FSM's present state.
  - ↳ Each state requires a unique bit encoding.
- Converting behavior (like an FSM) to a circuit is called design.
  - ↳ In contrast, converting a circuit to behavior is called analysis.
- Controllers inputs are typically the normal inputs AND the present state bits.
- Controllers outputs are typically the normal outputs AND the next state bits.
- Designers convert FSM to sequential circuit by first doing FSM  $\rightarrow$  truth table, then truth table  $\rightarrow$  equations, then equations  $\rightarrow$  combinational circuit



\*State encodings are in red

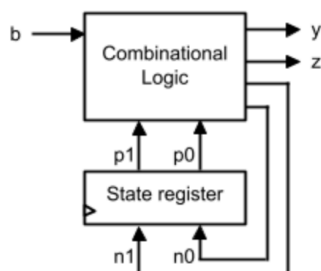

	p1	p0	b	n1	n0	y	z
s	0	0	0	1	0	0	1
	0	0	1	0	(F)	0	1
t	0	1	0	0	0	(C)	(D)
	0	1	1	1	0	0	(E)
u	1	0	0	(G)	0	1	0
	1	0	1	1	0	1	0
unused	1	1	0	0	0	0	0
	1	1	1	0	0	0	0

$$c = 0$$

$$d = 0$$


$$e = 0$$

$$f = 1$$

$$g = 0$$
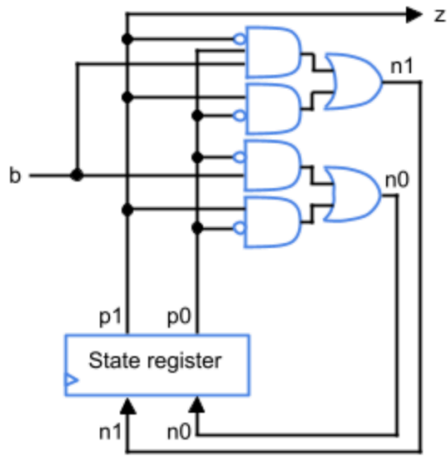
# 15.6 Circuits to FSMs (analysis)

• Converting from circuit to behavior (like an FSM) is called analysis.



p1	p0	b	n1	n0	z
0	0	0	0	0	(Q)
0	0	1	0	1	0
<hr/>					
0	1	0	(R)	(S)	0
0	1	1	(T)	0	0
<hr/>					
1	0	0	1	1	(U)
1	0	1	1	1	1
<hr/>					
1	1	0	0	0	1
1	1	1	0	0	1

$a = 0$

$r = 0$


$s = 0$

$t = 1$

$u = 1$

	p1	p0	b	n1	n0	z
e	0	0	0	0	0	0
	0	0	1	0	1	0
f	0	1	0	0	0	0
	0	1	1	1	0	0
g	1	0	0	1	1	1
	1	0	1	1	1	1
h	1	1	0	0	0	1
	1	1	1	0	0	1

Inputs: b  
Outputs: z

 

\*State encodings are in red

$m = 0$

$n = 1$

$P = b'$

$Q = b$

$R = e$

## 15.8 Clock Frequency

- A sequential system's clock frequency,  $f_c$ , cannot be arbitrarily fast.
  - ↳ registers could capture incorrect values.

- The critical path delay,  $t_c$ , for a sequential circuit is the longest propagation time through flip-flop outputs, through logic, then back to flip-flop data inputs.

↳ delay interval starts at the clock's active edge and ends at the flip-flop data input.

↳ the interval includes the flip-flop delay,  $t_{ff}$ , and combinational gate propagation delays,  $t_p$ .

$$t_c = t_{ff} + \max(\sum t_p)$$

- For proper operation, the clock period  $T$  must exceed the critical path delay:  $T > t_c$ .

- The clock frequency,  $f_c = 1/T$ , in Hz, is the inverse of clock period in seconds.

- In practice, designers typically increase the clock period by a "safety" margin of 10% to 30%. (Ex:  $T = 1.3 t_c$ )